

KATHMANDU UNIVERSITY
End Semester Examination
March, 2025

Marks Scored:

Level : B.Sc.

Year : II

Exam Roll No. :

Time: 30 mins.

Registration No.:

Course : EEEG 211

Semester : I

F. M. : 10

Date

24 MAR 2025

SECTION "A"

[20 Q. × 0.5 = 10 marks]

Choose and encircle the most appropriate option from each set of choices

1. Which type of extrinsic semiconductor is created when pentavalent impurities are added to pure silicon? _____
2. What is the main function of a Zener diode?
 - a. To rectify AC signal
 - b. To amplify signals
 - c. To regulate voltage
 - d. To switch circuits
3. What happens if a diode is reverse biased beyond its breakdown voltage?
 - a. It stops conducting permanently
 - b. It starts conducting heavily
 - c. It operates normally
 - d. It decreases resistance
4. A diode clipper circuit is used to limit the:
 - a. Frequency of a signal
 - b. Amplitude of a signal
 - c. Phase of a signal
 - d. Power of a signal
5. In a voltage divider bias circuit, what is the primary advantage?
 - a. Simplicity.
 - b. High stability of the Q-point.
 - c. Low cost.
 - d. High gain.
6. What is the purpose of a bypass capacitor in an emitter-biased amplifier?
 - a. To block DC signals.
 - b. To provide AC feedback.
 - c. To short AC signals to ground.
 - d. To increase DC gain.
7. Given an emitter-bias circuit with $V_{EE} = -10V$, $R_E = 2k\Omega$, and assuming $V_{BE} = 0.7V$, the emitter current (I_E) is _____ mA.
8. In AC small signal analysis, what happens to DC voltage sources?
 - a. They are replaced by open circuits.
 - b. They are replaced by short circuits.
 - c. They are doubled.
 - d. They remain the same.
9. A circuit designer needs a transistor with extremely high input impedance. Which of the following would be the most suitable choice, and why?
 - a. BJT, due to its high current gain.
 - b. JFET, because of its reverse-biased gate-source junction.
 - c. MOSFET, due to its insulated gate.
 - d. Any transistor, as input impedance is not a significant factor.

10. A JFET's drain current (I_D) saturates at a certain drain-source voltage (V_{DS}). What is the primary factor that limits the further increase of I_D with increasing V_{DS} in the saturation region?
 - a. The gate current.
 - b. The channel pinch-off.
 - c. The source resistance.
 - d. The ambient temperature.
11. Which amplifier is characterized by a low input impedance and a high output impedance?
 - a. Current amplifier.
 - b. Transresistance amplifier.
 - c. Voltage amplifier.
 - d. Transconductance amplifier.
12. The purpose of impedance matching is to:
 - a. Maximize voltage gain.
 - b. Maximize power transfer.
 - c. Minimize current gain.
 - d. Minimize signal distortion.
13. Why are push-pull configurations so often used in class B power amplifiers?
 - a. To increase the amplifiers class A operation.
 - b. To reduce even order harmonic distortion.
 - c. To decrease the total power output.
 - d. To increase the amplifiers input impedance.
14. Which class of amplifier operates for the entire input signal cycle?
 - a. Class A.
 - b. Class B.
 - c. Class C.
 - d. Class D.
15. What is the purpose of a comparator circuit using an op-amp?
 - a. To amplify the input signal
 - b. To compare two input voltages and provide a digital output
 - c. To integrate the input signal
 - d. To differentiate the input signal
16. What is the meaning of I_{DSS} in relation to JFETs?
 - a. Input Drain Source Signal.
 - b. Ideal Drain Source State.
 - c. Drain-to-Source current with Gate shorted to Source.
 - d. Indirect Drain Supply State.
17. In a half-wave rectifier, a capacitor is added in parallel with the load. What is the effect on the ripple voltage?
 - a. The ripple voltage increases.
 - b. The ripple voltage decreases.
 - c. The ripple voltage remains the same.
 - d. The ripple voltage becomes a square wave.
18. An amplifier has a gain of 40 dB. If the input signal power is doubled, the change in the output signal power (in dB) is _____.
19. A Zener diode is used in a voltage regulator circuit. If the load current increases significantly, what happens to the current through the Zener diode?
 - a. It increases.
 - b. It decreases.
 - c. It remains constant.
 - d. It becomes zero.
20. A circuit combines a diode bridge rectifier, a capacitor filter, and a Zener diode regulator. If the AC input voltage fluctuates significantly, which component primarily ensures a stable DC output voltage?
 - a. The diode bridge.
 - b. The capacitor filter.
 - c. The Zener diode.
 - d. All components contribute equally.